

# **ELEC 301 - Mini Project 1**

**Name: Nafeesa Nawar**

**Student ID: 33577735**


# Table of Contents

Question 1 - Part 1 .....	2
Question 1 - Part 2 .....	4
Discussion - question 1.....	6
Question 2 - Part 1 .....	6
Question 2 - Part 2 .....	8
Discussion - question 2.....	9
Question 3 - Part 1 .....	9
Question 3 - Part 2 .....	13
Discussion - question 3.....	14
References .....	15

## Question 1

### Question 1- Part 1

**Midband Gain:** In order to find the midband gain we open C2 and C3, short C1 and C4 and doing so we acquire the following circuit.

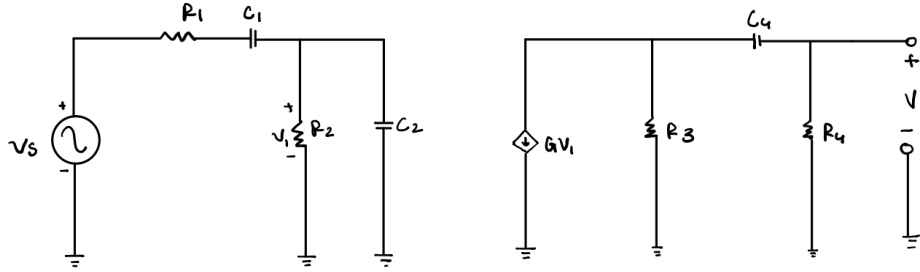

**Figure 1.1: Midband gain circuit**

Now, we can get the following equation from the above circuit and calculate the value for midband gain.

$$V_o = \frac{(-G_1)(V_1)(R_3 R_4)}{R_3 + R_4}$$


$$V_s = V_1 \left( \frac{R_1}{R_2} + 1 \right)$$

$$A_m = \frac{V_o}{V_s}$$

$$A_m = \frac{(-G_1)(R_3 R_4)}{(R_3 + R_4) \left( \frac{R_1}{R_2} + 1 \right)}$$

$$A_m = -195.12195122 \quad \frac{V}{V}$$

**Location of poles at low frequency:** At low frequency, C2 and C3 are open circuit which gives rise to the following circuit.

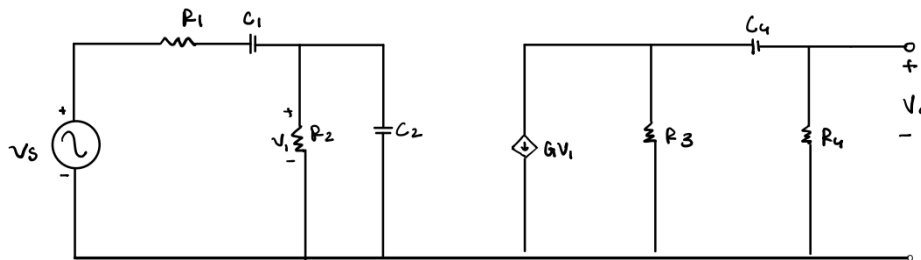

**Figure 1.2: Transconductance Amplifier at low frequency**

$$\omega_{LP1} = \frac{1}{(R_1 + R_2)C_1}$$

$$= 121.9512195 \text{ rad/s}$$


$$\omega_{LP2} = \frac{1}{(R_3 + R_4)C_4}$$

$$= 125 \text{ rad/s}$$

$$\omega_{13dB} = \sqrt{\omega_{LP1}^2 + \omega_{LP2}^2}$$

$$= 174.63418892 \text{ rad/s}$$

**Location of poles at high frequency:** At high frequency  $C_1$  and  $C_4$  are short circuits which gives rise to the circuit below.

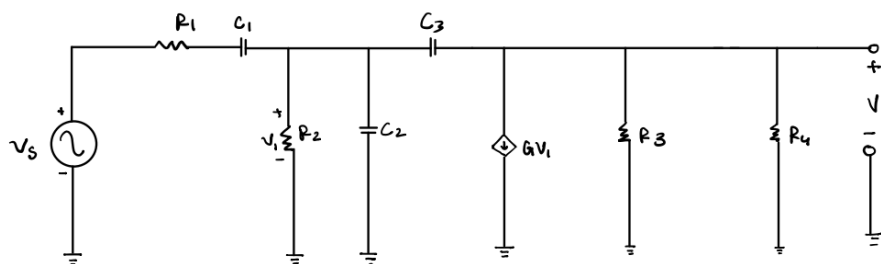


**Figure 1.3: Transconductance amplifier at high frequency**

From the above circuit in 1.4, we can find the miller gain  $k$  which gives rise to the circuit in figure 1.5.

$$k = \frac{v_o}{v_i} = (-G_1)(R_3 \parallel R_4)$$

$$= -200$$

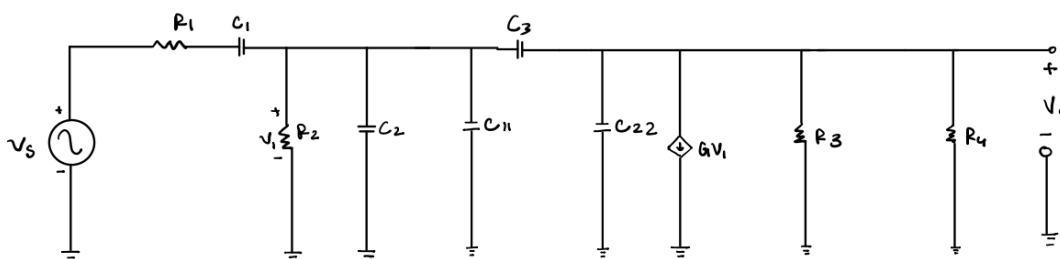

**Figure 1.4: Transconductance Amplifier at High frequency**

$$C_{11} = (1-k)C_3$$

$$= 0.000000000402 \text{ F}$$

$$C_{22} = C_3 \left( \frac{k}{1-k} \right)$$

$$= 2.01005025126 \times 10^{-12}$$

$$C_{22} = C_3 \left( \frac{k}{1-k} \right)$$

$$= 2.01005025126 \times 10^{-12}$$

$$\tau_1 = (C_2 + C_{11}) (R_1 \parallel R_2)$$

$$= 2.0097560975 \times 10^{-8} \text{ s}$$

$$= 49757281.5534 \text{ rad/s}$$

$$\tau_2 = (C_{22}) (R_3 \parallel R_4)$$

$$= 4.02010050251 \times 10^{-9} \text{ s}$$

$$= 248750000 \text{ rad/s}$$

$$\omega_{H3dB} = \frac{1}{\sqrt{(2.0098 \times 10^{-8})^2 + (4.0201 \times 10^{-9})^2}}$$

$$= 48790754.0884 \text{ rad/s}$$

### **Question 1 - Part 2**

Here we simulate the original circuit and probe it around  $V_o$  in order to plot the bode plot.



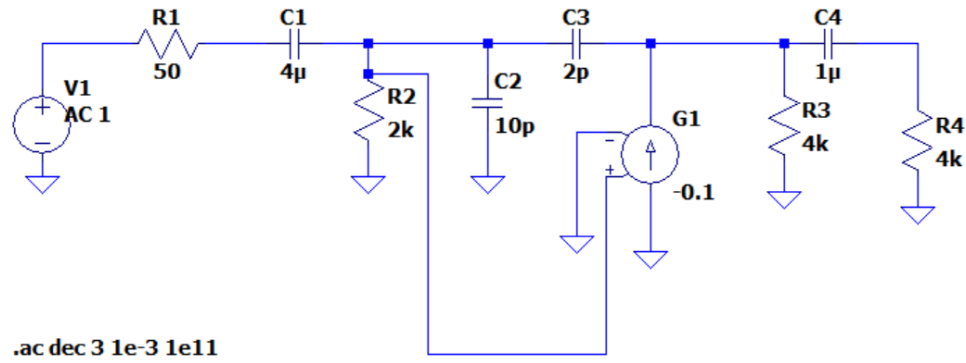


Figure 1.5: Simulated circuit for bode plot

### Magnitude Plot

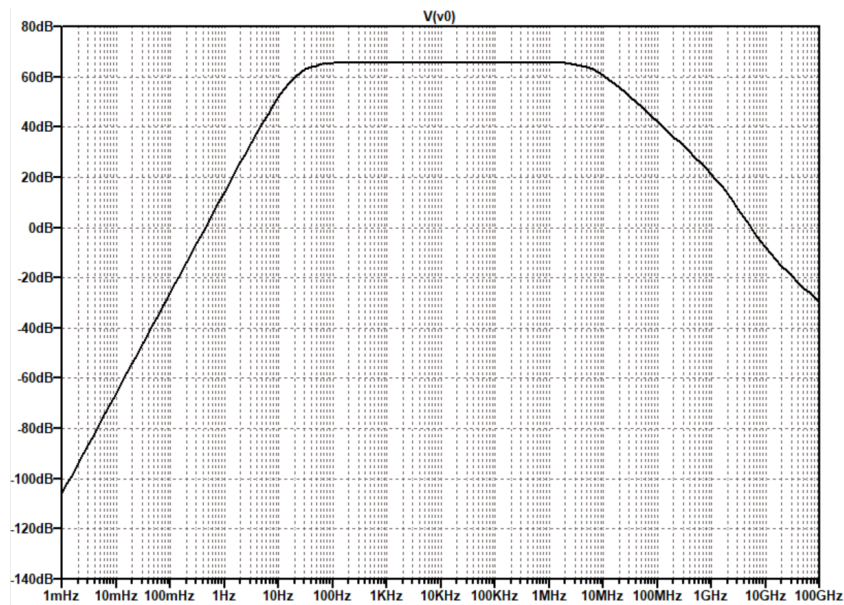

### Phase plot

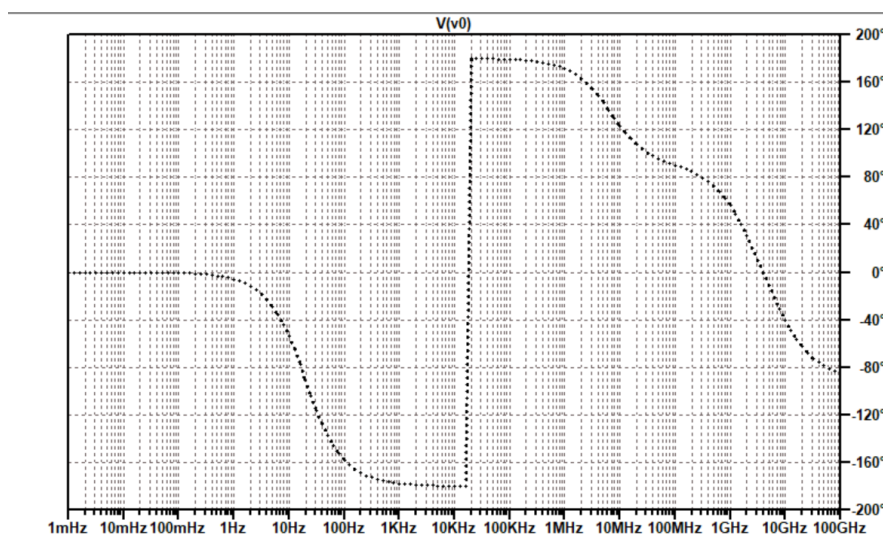

To determine the locations of our poles, we employ a variety of slopes, with their intersections indicating pole positions. Notably, this time, our plot reveals the presence of a

high-frequency zero. I sketched lines on the plot at the highest dB level, a slope of 40dB per decade, a slope of 20dB per decade, a slope of -40dB per decade, and two slopes of -20dB per decade. These lines were aligned on my bode plot, with the points of intersection indicating the positions of both poles and zeros.

**Table 1.1: Comparing Graphically Simulated Pole-Zero Values to Calculated Poles**

	$\omega_{lp1}$	$\omega_{lp2}$	$\omega_{h1}$	$\omega_{h2}$	$\omega_{z1}$
<b>Calculated rad/s</b>	121.9512	125	$49.7573 \times 10^6$	$25.1250 \times 10^8$	N/A
<b>Simulated rad/s</b>	123.9327	121.8812	$45.8675 \times 10^6$	$12.7651 \times 10^6$	$5.2131 \times 10^{10}$

We notice that low-frequency poles exhibit values that closely resemble each other. However, as we move to higher frequencies, we observe greater deviations among these values. Additionally, the high zero is no longer present when Miller's theorem is applied.

**Table 1.2: Determining Percent Error between Graphically Simulated and Calculated 3 dB Values**

	<b>Calculated (rad/s)</b>	<b>Simulated (rad/s)</b>	<b>% error</b>
$\omega_{L3dB}$	174.6342	192.9120	9.4747%
$\omega_{H3dB}$	48790754.0884	41698188.3885	17.0093%

We use the following equation to carry out the above percentage calculations:

$$\text{Error} = \frac{|\text{calculated} - \text{Simulated}|}{\text{Simulated}} \times 100$$

### Discussion:

As it can be seen from the above table, we notice that the error is relatively low at the lower 3 dB point, but it significantly escalates at the higher 3 dB point. The same trend is seen in the simulated values of poles versus the calculated values of poles. Therefore, it is safe to assume that any calculated pole values in higher frequency would have a higher percentage error and would not produce the most accurate result.

## Question 2

## Question 2 - part 1

### Magnitude Plot



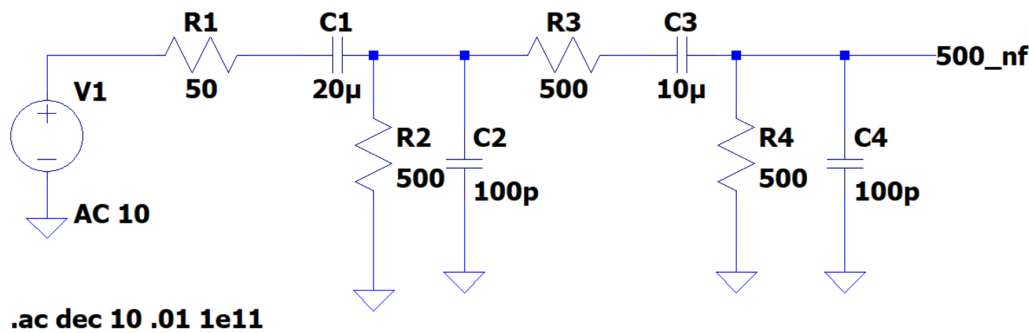


Figure: 2.1: Simulated circuit for bode plot

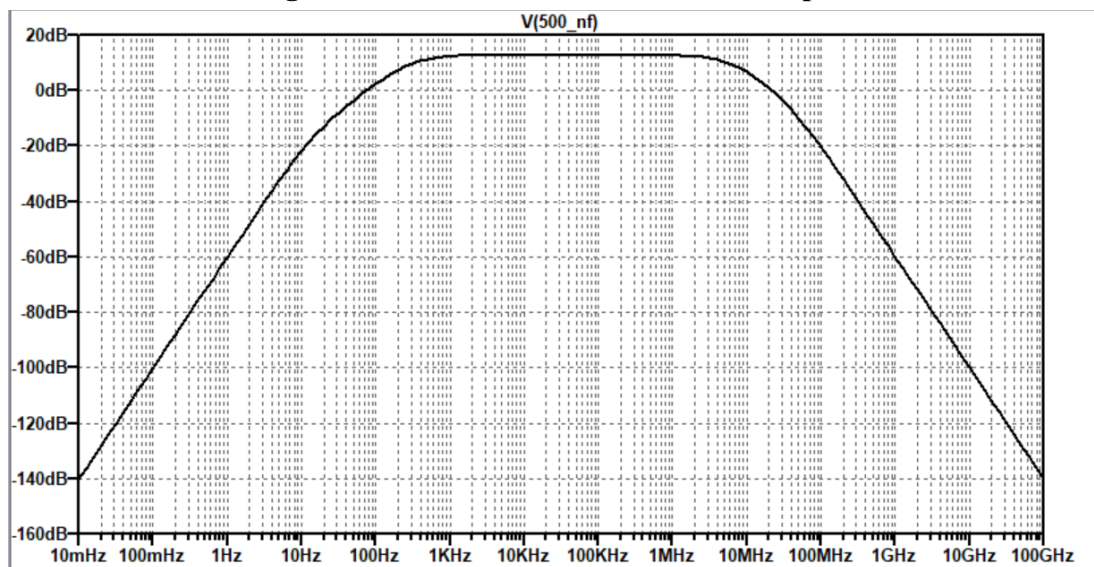

### Phase plot

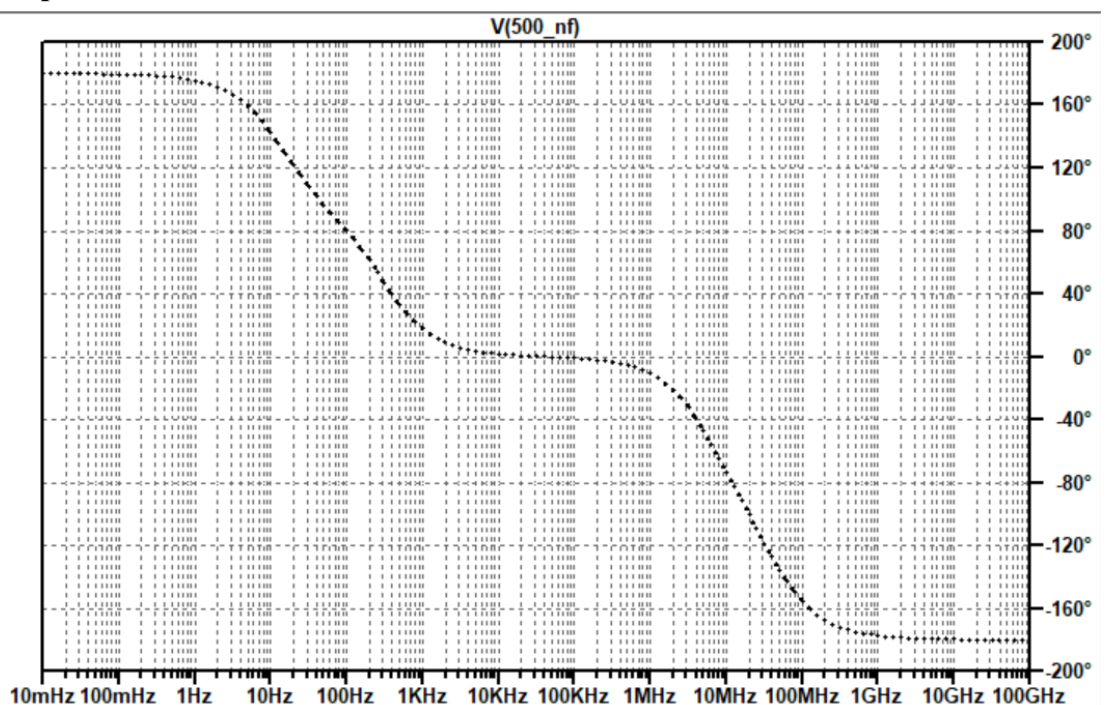



### Location of poles

I visually determined the pole positions by sketching lines that traversed the highest dB value, as well as lines with slopes of -20 dB/dec, -40 dB/dec, 20 dB/dec, and 40 dB/dec, aligning them with the magnitude plot. The initial pole was identified at the point where the -40 dB/dec and -20 dB/dec slopes intersected. The second pole was pinpointed at the intersection of the -20 dB/dec slope and the line representing the maximum value. A similar process was employed on the right side of the plot to ascertain the locations of the third and fourth poles.

**Table 2.1: Location of Poles**

Poles	Frequency (Hz)
$\omega_{lp1}$	15.1135 Hz
$\omega_{lp2}$	320.5673 Hz
$\omega_{lp3}$	5.10 MHz
$\omega_{lp4}$	41.7225 MHz

From graphically, it is also determined that the  $f_{L3dB}$  point is at 313.11365 Hz and the  $f_{h3dB}$  point is at 5.97729 MHz.

### Question 2 - Part 2

We solve for  $\omega_{LP1}$  by open circuit  $C_2$ ,  $C_3$  and  $C_4$  and calculating the resistance seen by  $C_1$ .

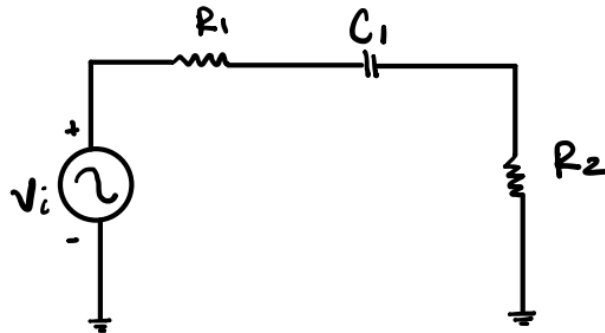


Figure 2.1: Circuit for finding  $\omega_{LP1}$

$$\omega_{LP1} = \frac{1}{(R_1 + R_2) C_1}$$

$$= 90.9091 \text{ rad/s}$$

We solve for  $\omega_{lp2}$  by short circuit  $C_1$  and open circuiting  $C_2$  and  $C_4$  and find the resistance seen by  $C_3$ . Then we find the  $\omega_{L3dB}$  value using the formula in [1].

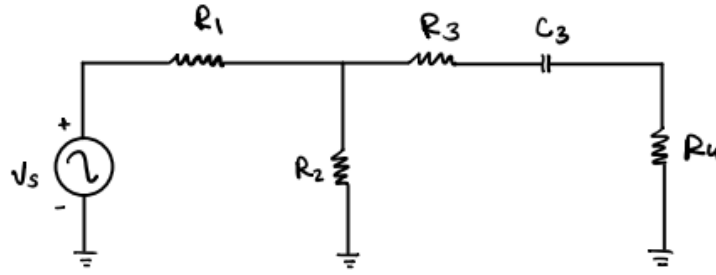


Figure 2.2: Circuit for finding  $W_{LP2}$

$$W_{LP2} = \frac{1}{(C_3) \left( \frac{1}{R_1} + \frac{1}{R_2} + R_3 + R_4 \right)}$$

$$= 1913.0435 \text{ rad/s}$$

$$W_{L3dB} = \sqrt{W_{LP1}^2 + W_{LP2}^2}$$

$$= 1915.2023 \text{ rad/s}$$

We follow the same process for the other capacitor values and acquire the following result:

Capacitor values	1 $\mu\text{F}$	2 $\mu\text{F}$	5 $\mu\text{F}$	10 $\mu\text{F}$
Calculated $W_{LP1}$ values	90.901 rad/s	90.901 rad/s	90.901 rad/s	90.901 rad/s
Calculated $W_{LP2}$ values	956.5218 rad/s	478.2609 rad/s	191.3043 rad/s	95.6522 rad/s
Simulated $W_{LP1}$ values	84.6513 rad/s	68.1657 rad/s	51.2523 rad/s	36.1471 rad/s
Simulated $W_{LP2}$ values	1102.4729 rad/s	607.9885 rad/s	607.8763 rad/s	227.8746 rad/s
$W_{L3dB}$ Values	960.8321 rad/s	486.8243 rad/s	211.8061 rad/s	131.9614 rad/s

**Table 2.2: Calculated and simulated poles for different values for  $C_3$**

We use the following equation to calculate error:

$$\text{Error} = \frac{|\text{calculated} - \text{Simulated}|}{\text{Simulated}} \times 100$$

Capacitor Values	Calculated $W_{L3dB}$ rad/s	Simulated $W_{L3dB}$ rad/s	Error %
500 nF	1915.2023	1967.3232	2.6493
1uf	960.8321	1010.6146	4.9260
2 uf	486.8243	543.0436	10.3526
5 uf	211.8061	272.4714	22.2648
10 uf	131.9614	189.5995	30.39910

**Table 2.3: Percentage error for calculated and simulated  $W_{L3dB}$  values for different  $C_3$  values**

#### Discussion:

From the above calculation and simulation of plots, we can see that the circuit is a bandpass filter and the percentage of error increases as the values values of  $C_3$  increases.

### Question 3

#### Question 3 - Part 1

In order to solve this problem, we first need to find the values of the resistor. We know that four of the resistors have a value of  $750 \Omega$  and two of the  $1.5 \text{ k}\Omega$  values. We can achieve this by leveraging the provided mid-band gain of 0.125. Given that there are three nodes in the circuit, we can conclude that each node or voltage ratio will exhibit a gain of  $(0.125)^{1/3} = 0.5$ . Therefore we can split the midband gain as the following:

$$A_m = \frac{V_o}{V_2} \times \frac{V_2}{V_1} \times \frac{V_1}{V_s}$$

Since each voltage ratio have a gain of 0.5 and we are working in the midband all the high-frequency capacitors would have to be open circuit and all the low-frequency capacitors would have to be short circuits. Since this problem only has high-frequency capacitors, opening them would give rise to the following circuit:

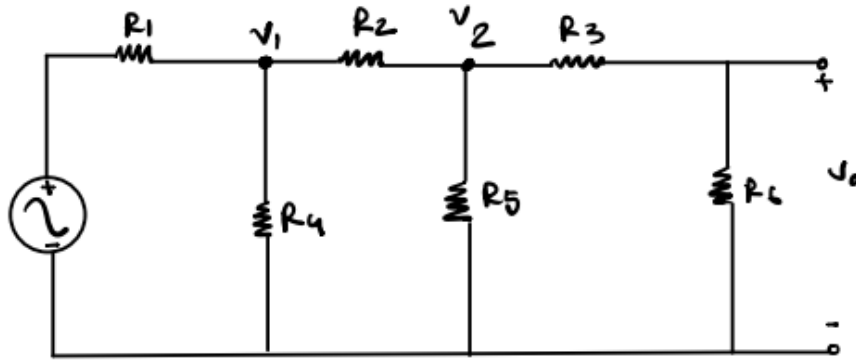


Figure 3.1: Midband Gain Circuit

$$\frac{V_o}{V_2} = \frac{R_6}{R_3 + R_6} = \frac{1}{2} \Rightarrow R_3 = R_6$$

$$\frac{V_2}{V_1} = \frac{R_5 \parallel (R_3 + R_6)}{R_2 + R_5 \parallel (R_3 + R_6)} = \frac{1}{2}, \quad \Rightarrow R_2 = \frac{2R_5R_6}{R_5 + 2R_6}$$

$$\frac{V_1}{V_s} = \frac{R_4 \parallel (R_2 + R_5 \parallel (R_3 + R_6))}{R_1 + R_4 \parallel (R_2 + R_5 \parallel (R_3 + R_6))} = \frac{1}{2} \Rightarrow R_1 = \frac{2R_2R_4}{2R_2 + R_4}$$

$$R_3 = 750 \, \Omega, \quad R_6 = 750 \, \Omega, \quad R_2 = 750 \, \Omega, \quad R_1 = 750 \, \Omega \\ R_5 = 1500 \, \Omega, \quad R_4 = 1500 \, \Omega$$

With our resistor values identified, we can proceed to ascertain the capacitor values using the OC and SC time constant method. Given the hierarchy of capacitor values, where  $C_1 > C_2 > C_3$ , we apply short-circuiting to capacitors with higher values than the one for which we are determining the OC time constant. Conversely, for capacitors with lower values (OC time constant, as these pertain to high-frequency capacitors), we open circuit them.

For finding  $C_1$ , we open circuit  $C_2$  and  $C_3$  and find the equivalent resistance seen by  $C_1$ .

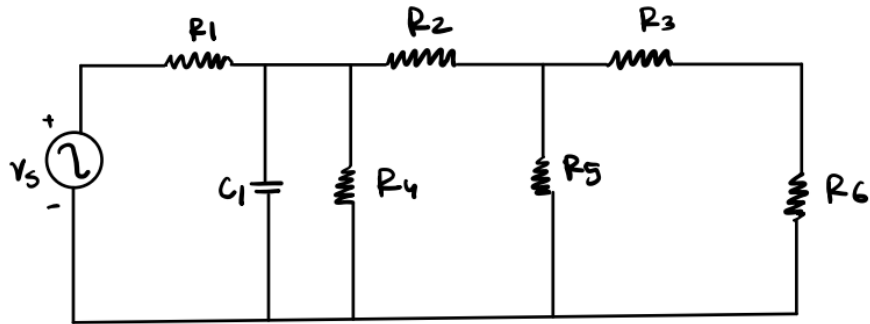


Figure 3.2: Circuit for finding  $C_1$

$$\omega_{P1} = \frac{1}{(C_1)(R_{eq})} = \frac{1}{(C_1)(R_1 \parallel (R_4 \parallel (R_2 + R_5 \parallel (R_3 + R_6))))}$$

$$C_1 = \frac{1}{(\omega_{P1})(R_{eq})} = 26.6667 \text{ nF}$$

For finding  $C_2$ , we short circuit  $C_1$  and open circuit  $C_3$  and find equivalent resistance seen by  $C_2$ .

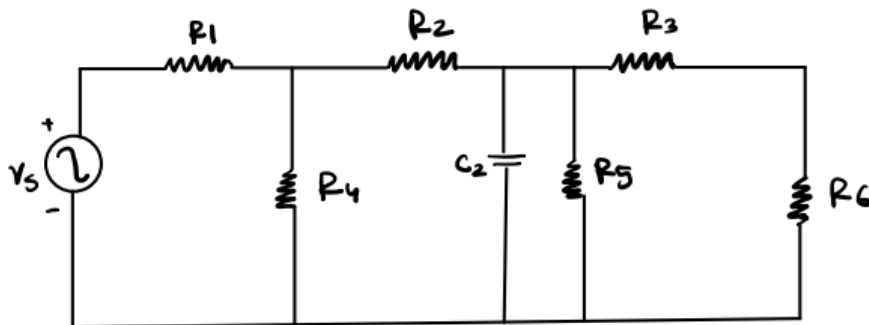


Figure 3.3: Circuit for finding  $C_2$

$$\omega_{P2} = \frac{1}{(C_2)(R_{eq})} = \frac{1}{(C_2)(R_2 \parallel (R_5 \parallel (R_3 + R_6)))}$$

$$C_2 = \frac{1}{(\omega_{P2})(R_{eq})} = 2.666 \text{ nF}$$

For  $C_3$ , we short circuit  $C_1$  and  $C_2$  and find equivalent resistance seen by  $C_2$ .

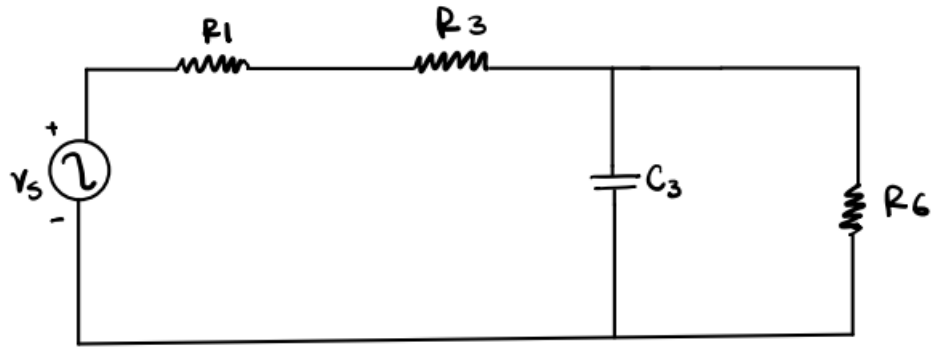


Figure 3.4: Circuit for finding  $C_3$

$$\omega_{p3} = \frac{1}{(C_3)(R_{eq})} = \frac{1}{(C_3)(R_3 || R_6)}$$

$$C_3 = \frac{1}{(\omega_{p3})(R_{eq})} = 266.66 \text{ pf}$$



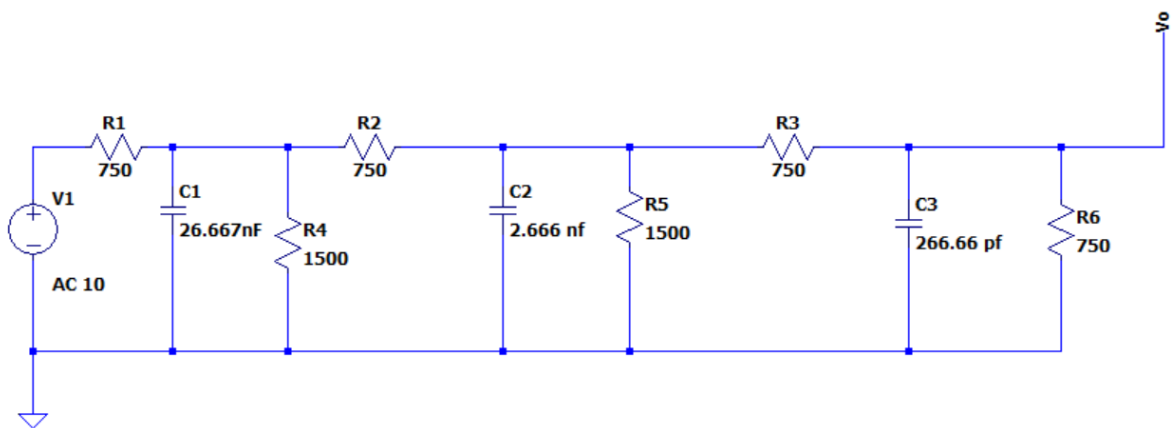


Figure 3.5: Simulated Circuit for plots

## Magnitude Plot

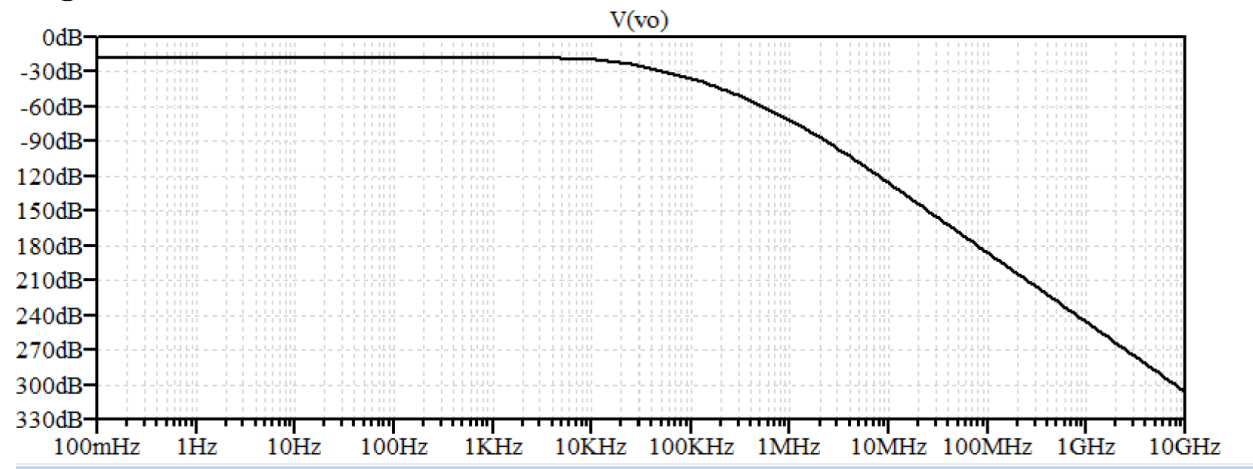

## Phase plot

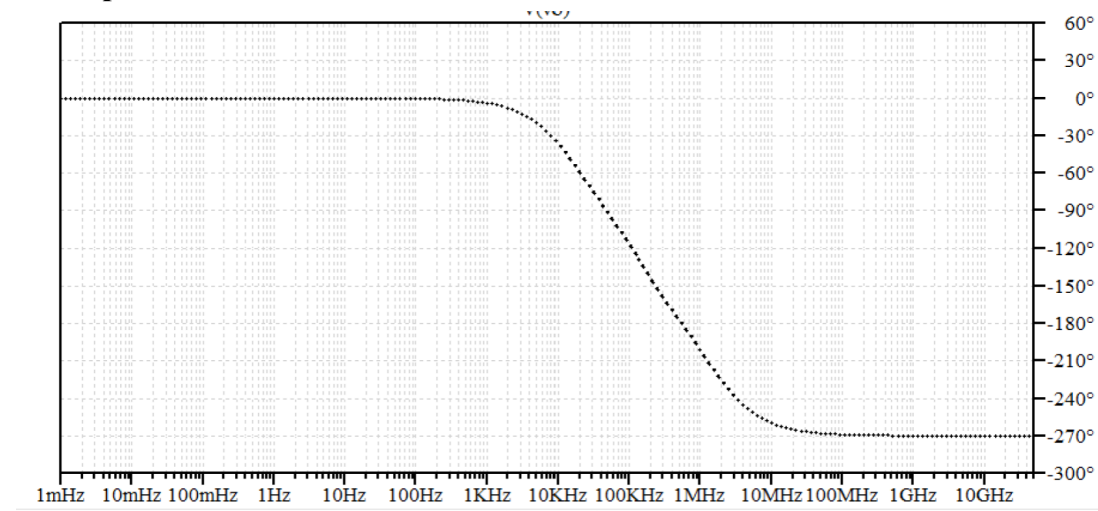

## Question 3 - Part 2



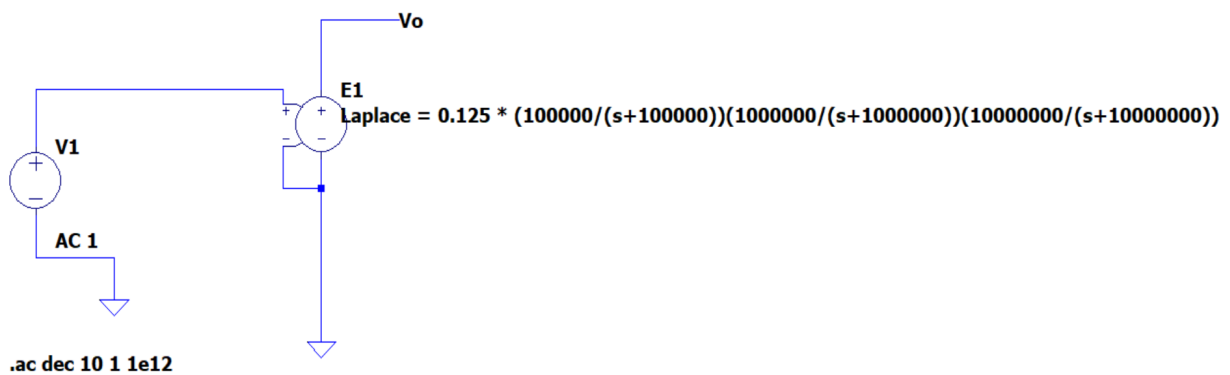


Figure 3.6: Simulated Laplace circuit

## Magnitude plot

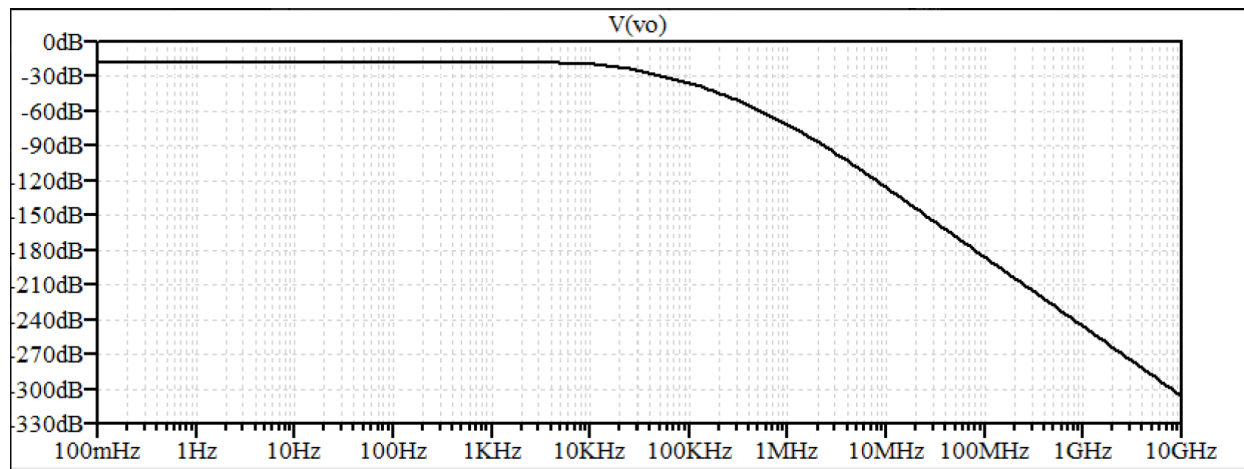

## Phase Plot:

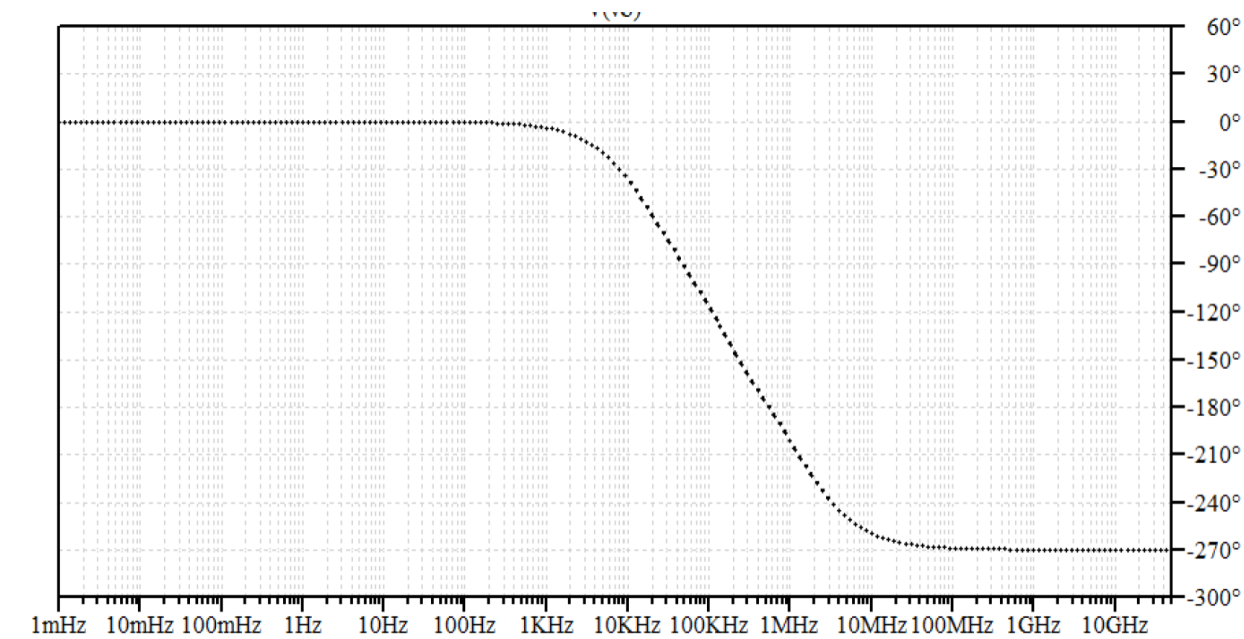

## Discussion:

Upon analyzing the Bode plots of the circuit in both part 1 and part 2, it becomes evident that the magnitude and phase plots exhibit an exceptionally close resemblance. This serves as compelling evidence that the transfer function serves as an exceptionally accurate mathematical approximation and model for the system.

## References

- [1] ELEC 301 Course Notes.
- [2] A. Sedra and K. Smith, "Microelectronic Circuits," 5<sup>th</sup> (or higher) Ed., Oxford University Press, New York.
- [3] LTSPICE™ User's Manual