

**Mini Project 4**  
**Nafeesa Nawar**  
**Student ID: 33577735**

**Table of Contents**

<b>Part A</b>	<b>2</b>
<b>Part B</b>	<b>5</b>
<b>Part C</b>	<b>9</b>
<b>References</b>	<b>17</b>

### Part A - An Active Filter

1)

Below we have shown the calculation of C and  $A_M$  that will turn the filter into a 2nd order Butterworth filter and give the filter a 3dB frequency of 10kHz.

$$C = \frac{1}{2\pi f_{3dB} R} = \frac{1}{(2\pi)(10\text{kHz})(10\text{k}\Omega)} = 1.5915 \text{ nF}$$

The transfer function given is:

$$H(s) = A_M \frac{1/(RC)^2}{s^2 + s \frac{3-A_M}{RC} + \frac{1}{(RC)^2}}$$

$$\text{We know, } s^2 + 2\zeta\omega_n s + \omega_n^2 = s^2 + s \frac{3-A_M}{RC} + \frac{1}{(RC)^2}$$

$$\text{Thus, } \zeta = \frac{3-A_M}{2} \quad \omega_n = \frac{1}{RC}$$

The normalized characteristic equation of a 2nd order butterworth filter is:  $s^2 + \sqrt{2}s + 1$ . This is because it has poles  $45^\circ$  from the real axis.

$$\text{Now, } A_M = 3 - \sqrt{2} = 1.5858 \text{ V/V}$$

Solving for  $R_1$  and  $R_2$  we get.

$$A_M = 1 + \frac{R_2}{R_1} \quad R_1 + R_2 = 10\text{k}\Omega$$

$$R_1 = 6306.0194 \Omega \quad R_2 = 3693.9806 \Omega$$

Using the values obtained above, the following circuit was simulated to achieve its bode plots.

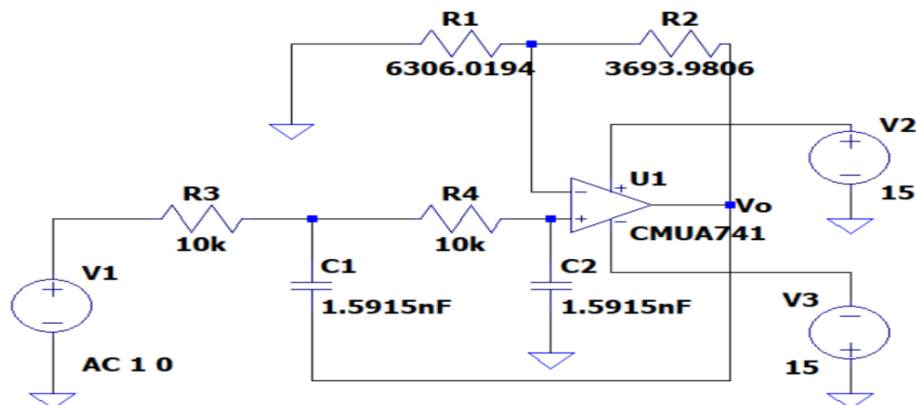


Figure 1.1: Simulated Circuit for bode plot

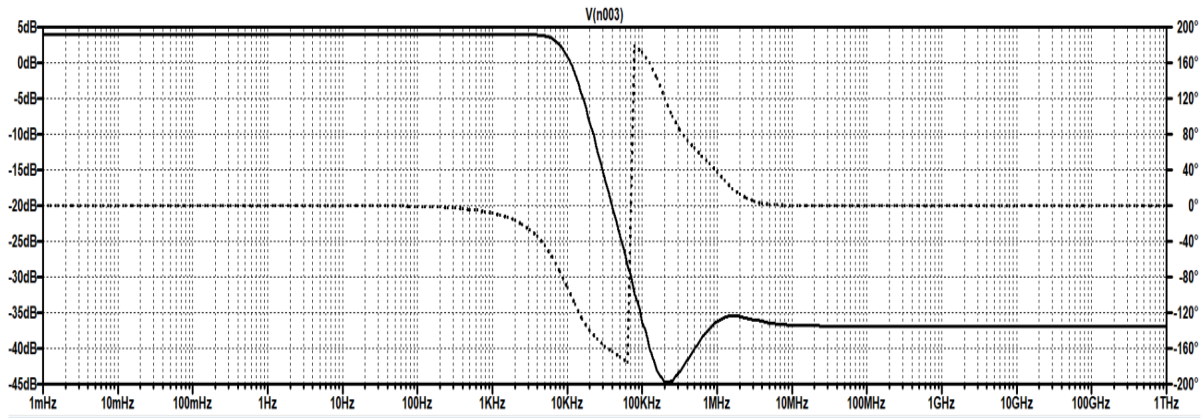


Figure 1.2: Magnitude and phase plot

From the simulation we have found the  $f_{3dB}$  to equal to 9.9776554 kHz. This is very close to the given of 10 kHz, proving the accuracy of our calculation.

Using the obtained values, below, we have shown where the poles in the S-plane. The simulation was done using matlab and two complex conjugate poles(  $-44.5k + 44.5j$  and  $-44.5k - 44.5j$  ) was obtained.

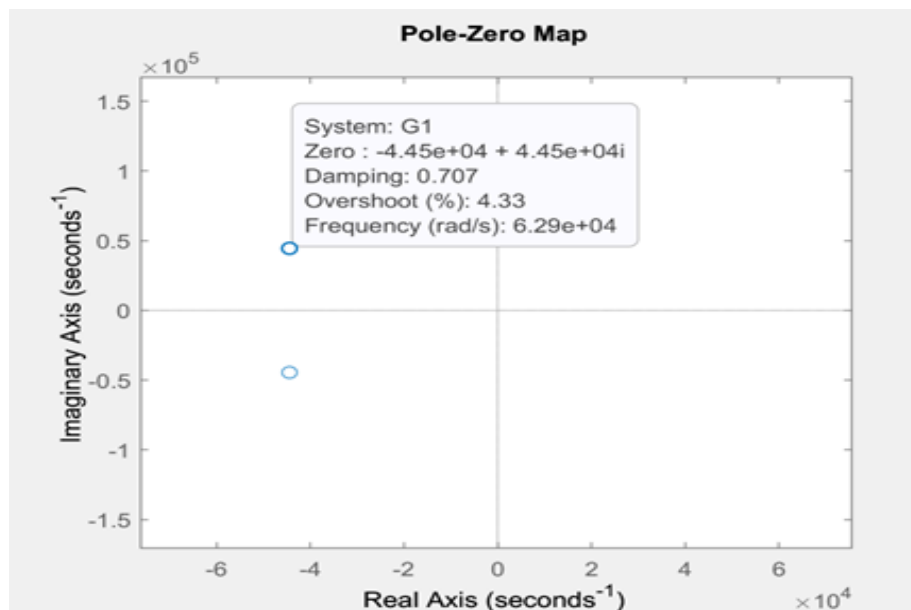


Figure 1.3: Pole-zero Map

2)

In figure 1.4, 1.5 and 1.6, we have depicted the root locus graph for  $A_M < 3$ ,  $A_M = 3$  and  $A_M > 3$ . Note that when  $A_M = 3$ , the  $s$  term of the transfer function disappears and our pole lies on the imaginary axis, meaning  $s = \pm j(1/RC)$ . In figure 1.5 and 1.6  $A_M$  goes from greater than 3 to 3. When that happens the poles travel from the RHS of the  $s$  plane to the imaginary axis. Then again, when  $A_M$  goes from 3 to less than 3, the poles travel from imaginary axis to LHS of the  $s$  plane.

Therefore, in order for our system to oscillate, we need to ensure that  $A_M$  is greater than or equal 3. This will ensure our poles to be on RHS of the complex plane such that there is no exponential decay that can get rid of the oscillation. When  $A_M$  is less than 3, we observe

stable root locus plot. When  $A_M$  is greater than 3 the root locus plot is unstable and the characteristic equation is negative which causes instability and allow the system to oscillate.

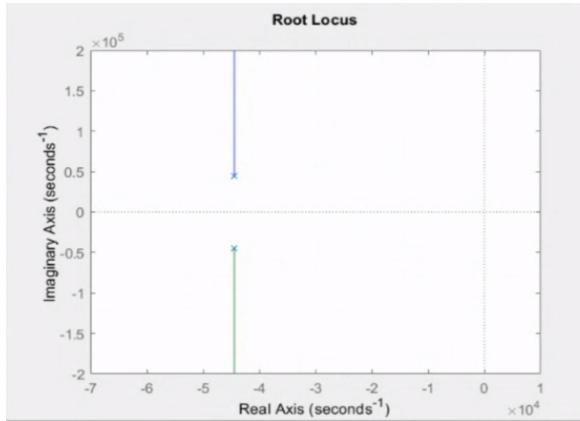


Figure 1.4:  $A_M < 3$

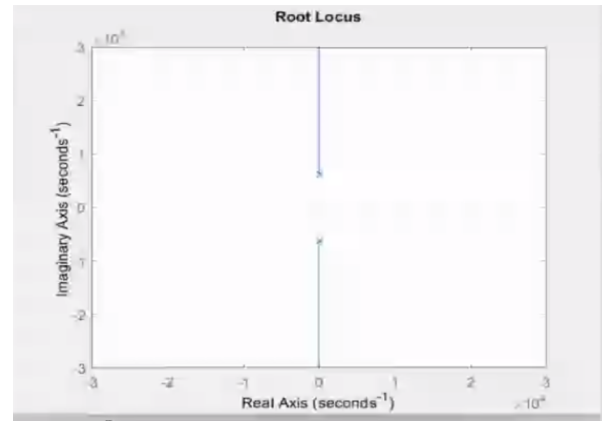


Figure 1.5:  $A_M = 3$

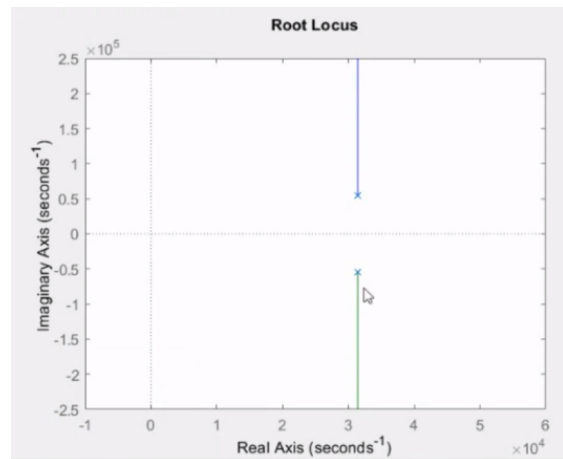


Figure 1.6:  $A_M > 3$

As mentioned above oscillation start to occur when  $A_M = 3$ . Thus, let us choose  $A_M = 3$  and observe the output. When  $A_M = 3$ ,  $R_1 = 3.3333 \text{ k}\Omega$  and  $R_2 = 6.6667 \text{ k}\Omega$ . In this way, we kept the value of  $R_1 + R_2 = 10 \text{ k}\Omega$  and changed the value of  $R_1$  and  $R_2$  in order to increase  $A_M$ . Now we can observe the output by subbing in the new  $R_1$  and  $R_2$  values.

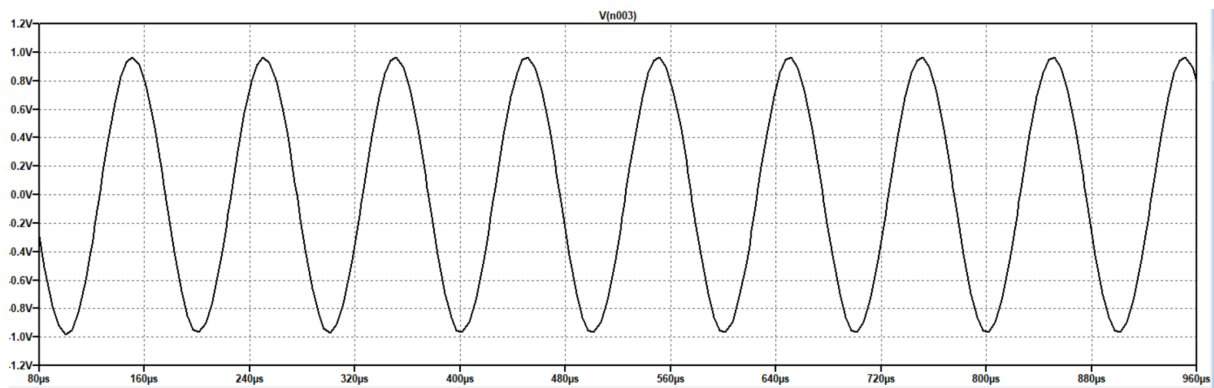


Figure 1.7: Oscilated output via grounding input

Via measuring the differences between the crest of the plot, the oscillating frequency was found to be  $f_o = 9.01 \text{ kHz}$ .

### Discussion:

In this segment, we crafted a second-order Butterworth filter in accordance with the provided specifications. Upon revisiting the denominator of our transfer function, it becomes evident that when the term involving 's' raised to the power of 1 is multiplied by zero, the function's poles assume a purely imaginary nature. This signifies an anticipated response characterized by continuous oscillation without decay. Consequently, we foresaw oscillations in the filter when  $A_M$  equals 3 V/V, with resistors R1 set at 3.3333k $\Omega$  and R2 at 6.6667k $\Omega$ . To delve deeper into this oscillatory behavior, an examination of the root locus reveals that an increase in  $A_M$  drives the poles towards the j $\omega$ -axis, resulting in purely imaginary poles and, consequently, inducing oscillations.

### Part B - A Phase Shift Oscillator

For this part of the project, we will analyse a phase shift oscillator depicted in figure 2.1. The oscillator comprises a feedback network with capacitors and resistors that induce a shift in the output. It also employs a feedback network with poles positioned on the j $\omega$ -axis and generates a phase shift proportional to its frequency. The transfer function of the feedback circuit is the following:

$$A_f = \frac{A}{1 + A\beta}$$

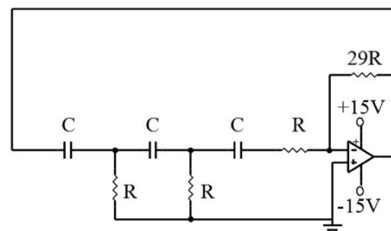


Figure 2.1: Phase Shift Oscillator

In order for the circuit to oscillate with a specific frequency of  $\omega_o$  without requiring an input,  $A_f$  would need to equal to infinity and  $A\beta$  need to equal to -1. In such a case, the complex conjugate poles would be located on the j $\omega$ -axis.

As mentioned in the question description, the values of R were chosen to be 1 k $\Omega$  and the values of C were 1  $\mu$ F. As mentioned in the question, the values of 29R had to be slightly higher, thus, a value of 29.3 k $\Omega$  was chosen.

The following equations below predicts the oscillating frequency of the circuit shown in figure 2.1 and then compared to the equations given in the class handouts.

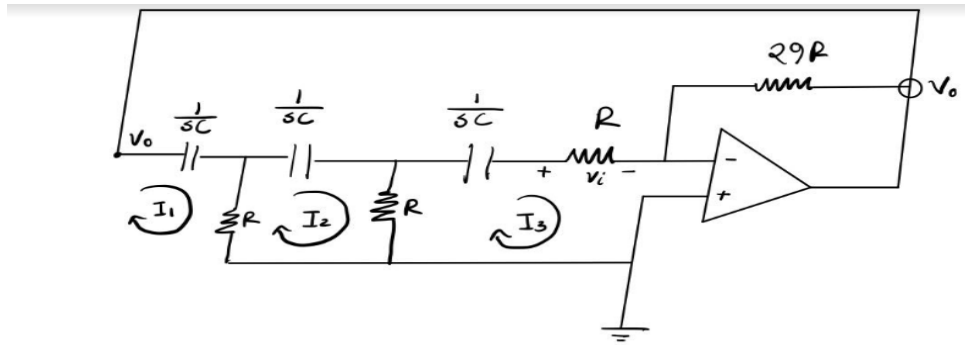


Figure 2.2: Circuit diagram with marked current to predict the equation for oscillating frequency

$$k = \text{gain} = \frac{V_o}{V_i}$$

$$k V_i = \frac{1}{sC} I_1 + R(I_1 - I_2) \longrightarrow \textcircled{1}$$

$$R(I_2 - I_1) + \frac{1}{sC} I_2 + R(I_2 - I_3) = 0 \longrightarrow \textcircled{2}$$

$$R(I_3 - I_2) + \left(\frac{1}{sC} + R\right) I_3 = 0 \longrightarrow \textcircled{3}$$

Solving for  $I_1, I_2, I_3$  we get:

$$I_3 = \frac{V_i}{R}$$

$$I_2 = \frac{V_i}{R} \left( \frac{1 + 2(sRC)}{sRC} \right)$$

$$I_1 = \frac{1}{R} \left( V_i \left( \frac{1 + 2(sRC)^2}{(sRC)^2} - 1 \right) \right)$$

Using  $I_1$ ,  $I_2$  and  $I_3$ , we solve for  $k$ .

$$kV_i = \frac{1+SRC}{SRC} \left( \frac{(1+2(SRC)^2)-1}{(SRC)^2} \right) V_i - R \left( \frac{V_i}{R} \left( \frac{1+2(SRC)}{(SRC)} \right) \right)$$

thus,

$$k = \frac{[(\omega RC)^3 - 5(\omega RC)] + j(1 - 6(\omega RC)^2)}{(\omega RC)^3}$$

By substituting gain to unity and the phase to  $180^\circ$ , the following equations were obtained which are same as class handouts.

$$f = \frac{1}{2\pi\sqrt{6}RC}$$

and

$$k = -29$$

Using the obtained equation for  $f$ , the oscillation frequency is calculated and listed below in the table. Using LTSpice, the output frequency was measured. The process was then repeated by doubling the value of  $R$  and  $C$  and halving the value of  $R$  and  $C$ . All the results obtained are summarised in table 2.1.

<b>R and C</b>	<b>Calculated f (Hz)</b>	<b>Measured f (Hz)</b>
1 k $\Omega$ , 1 $\mu$ F	64.97	64.29
2 k $\Omega$ , 2 $\mu$ F	16.24	16.16
0.5 k $\Omega$ , 0.5 $\mu$ F	259.90	257.89

Table 2.1: measured and calculated output frequencies

As seen from table 2.1, the calculated and measured frequencies are fairly close to one another which further proves the accuracies of the formulas used to predict the oscillating frequencies.



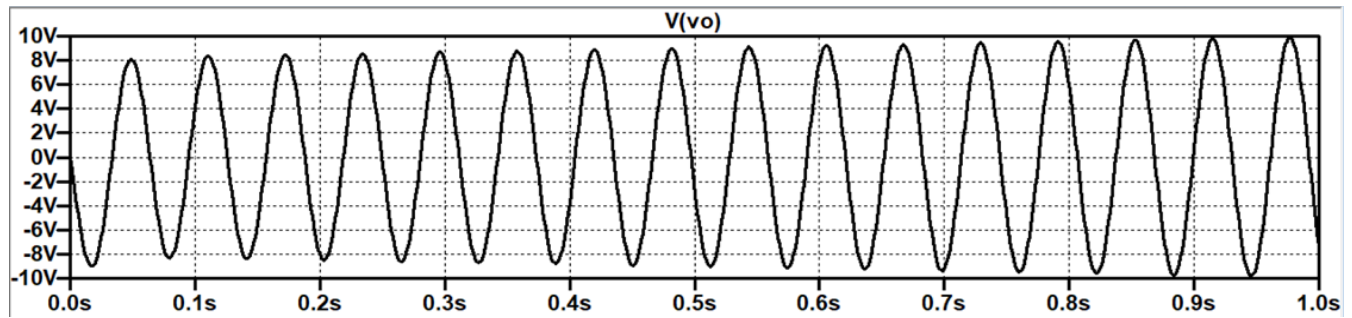


Figure 2.3: Oscillation for Doubled R and C

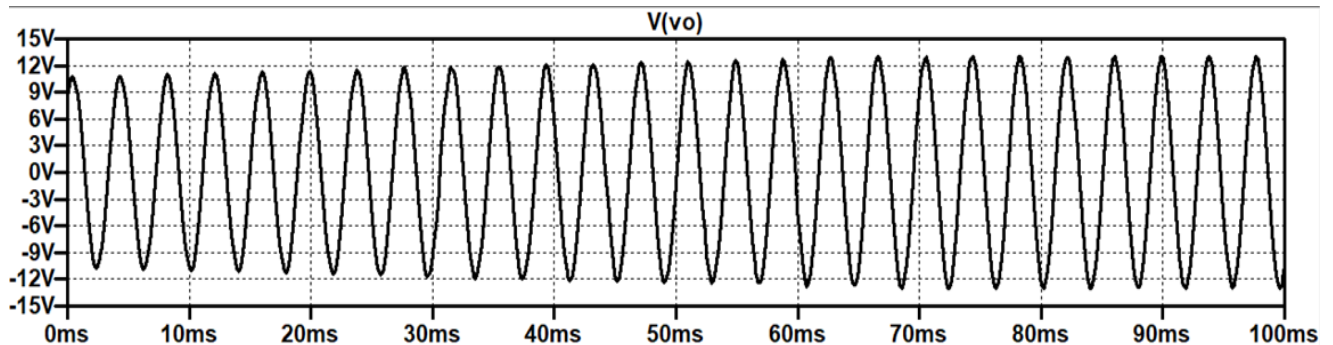


Figure 2.3: Oscillation for Halved R and C

### How a phase-shift oscillator works and why we had to increase the 29R resistor:

A Phase Shift Oscillator operates by leveraging feedback through an RC network to generate a sinusoidal waveform. It involves the cascading of three passive high-pass filter stages. Each of these filter stages contributes a phase shift of  $60^\circ$ , resulting in a cumulative phase shift of  $180^\circ$ . This contribution is then augmented by the  $-180^\circ$  introduced by the negative feedback from the amplifier. The net effect is a total phase shift of  $0^\circ$  in the transfer function, aligning with the Barkhausen criterion necessary for sustained oscillations.

Our calculations indicated that the operational amplifier necessitates a minimum gain of -29, aligning with the initial design of 29R and R for the inverting operational amplifier.

Nevertheless, to regulate the oscillation amplitude, we had to make a slight adjustment to the 29R value to ensure that  $|A\beta|$  is slightly greater than 1, causing the poles to shift to the right-hand plane for exponential growth and initiating oscillations. This condition was achieved by increasing the value from 29k to 29.3k.

### Discussion:

In this segment, we elaborate on the effective emulation of a phase-shift oscillator employing three distinct combinations of resistor and capacitor parameters. Previously, we delved into the fundamental principles governing oscillators and their mathematical application to phase-shift oscillators. Finally, our formula aligns with the lecture notes, yielding precise results. As depicted in Table 2.1, the computed and simulated values closely correspond. Additionally, we note an inverse relationship between the resistor and capacitor values and the oscillation frequency, in accordance with the deduced equation.

### Part C - A Feedback Circuit

In this section, we will analyse a feedback circuit comprising a common emitter stage succeeded by a common collector stage serving as our amplifier. The feedback network employs a resistor. Given that we measure voltage at the output and feeding back a current to the input, we can utilise y-parameters, as this configuration aligns with a shunt-shunt topology.

Initiating the amplifier biasing process is our first step. To create the largest open-loop gain at 1kHz, the crucial task is selecting the appropriate value for  $R_{B2}$ . By disconnecting  $R_f$  in figure 3.1 and observing the magnitude bode plot at 1kHz, we can explore various  $R_{B2}$  values to identify the one that yields the highest gain. Below, the observed gains and the values of  $R_{B2}$  is recorded in table 3.1.

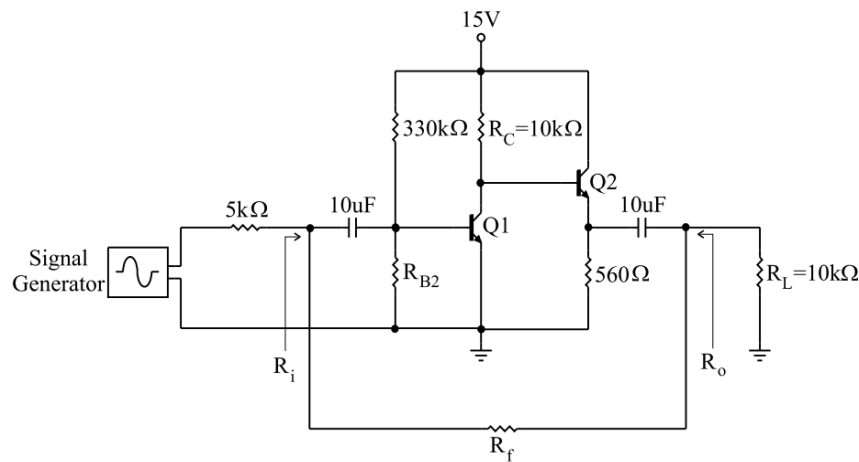


Figure 3.1: The Feedback circuit

$R_{B2}$ Value (k $\Omega$ )	1	10	15	20	25	30	35
Gain (dB)	-98.8	-23.7	33.5	42.1	-95.9	-10e1.3	-104.2

Table 3.1: Different Values of  $R_{B2}$  at 1 kHz and Open Loop Gain

From table 3.1, we can notice that the gain is when  $R_{B2}$  is around 20 k $\Omega$ . Thus,  $R_{B2} = 20$  k $\Omega$ .

1)

The DC operating point feature in LTspice is used to obtain the DC operating values for both the transistors and listed in table 3.2

	$I_C$ (mA)	$I_B$ ( $\mu$ A)	$I_E$ (mA)	$V_C$ (V)	$V_B$ (V)	$V_E$ (V)
Q1	1.29	10.81	1.31	1.90	0.65	0
Q2	2.19	15.432	2.22	15	1.90	1.23

Table 3.2: DC Operating Points

Using the obtained values in 3.1, the values of  $h_{FE}$ ,  $g_m$  and  $r_{\pi}$  is calculated below.

$$(V_T = 25 \text{ mV})$$

$$g_{m1} = \frac{I_{C1}}{V_T}$$

$$= 51.6 \text{ mS}$$

$$r_{\pi1} = \frac{V_T}{I_{B1}}$$

$$= 2312.67 \Omega$$

$$h_{FE1} = (r_{\pi1})(g_{m1})$$

$$= 119.33$$

$$g_{m2} = \frac{I_{C2}}{V_T}$$

$$= 87.6 \text{ mS}$$

$$r_{\pi2} = \frac{V_T}{I_{B2}}$$

$$= 1620.01 \Omega$$

$$h_{FE2} = (r_{\pi2})(g_{m2})$$

$$= 141.91$$

2)

Keeping  $R_f$  to an open circuit the as in part 1, the bode plot is depicted in figure 3.2 and the values were obtained in table 3.3. The input and output resistances were measured using a voltage and current test source.

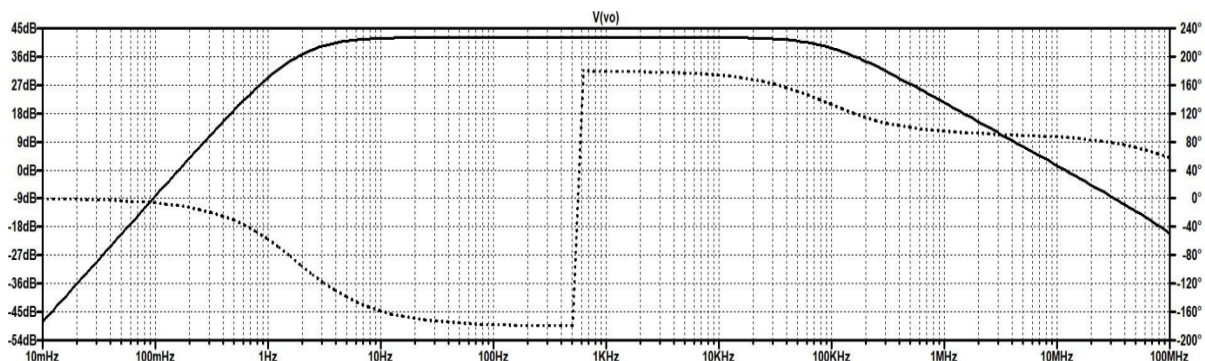


Figure 3.2: Bode plot for open loop

$F_{L3dB}$	$F_{H3dB}$	$R_{in}$	$R_{out}$	Open loop Gain ( $A_M$ )
2.94 Hz	90.31 kHz	2.57 k $\Omega$	62.13 $\Omega$	42.11 dB/ -125.55 V/V

Table 3.3:  $F_{L3dB}$ ,  $F_{H3dB}$ ,  $R_{in}$ ,  $R_{out}$  and Open Loop Gain

The open-loop frequency response found above is used to calculate the following values: the predicted closed-loop frequency response and both the input and output resistance at 1kHz of our amplifier for  $R_f = 100 \text{ k}\Omega$ . The calculation is shown below. Since the amplifier we are using is a shunt-shunt configuration, we use y-parameters for our calculations.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$\beta = y_{12} \quad I_1 = y_{11}V_1 + y_{12}V_2$$

$$\left( \begin{array}{l} y_{12} = \frac{I_1}{V_2} \\ V_1 = 0 \end{array} \right) = \frac{-1}{R_F} = \beta = -10 \mu\Omega$$

Open loop gain can be shown in terms of output voltage over input current as we have a shunt-shunt topology.

$$\begin{aligned} A' &= \frac{V_o}{I_s} = R_s \left( \frac{V_o}{V_s} \right) = (-126.3 \frac{V}{V}) (5k\Omega) \\ &= -631.6 \frac{kV}{A} \end{aligned}$$

closed loop gain,  $A_F$ :

$$A_F = \frac{A'}{1 + A'\beta} = -86.33 \frac{kV}{A}$$

closed loop input and output resistances

$$R_{in, closed} = \frac{R_{in, open}}{1 + A'\beta} = 352 \Omega$$

$$R_{out, closed} = \frac{R_{out, open}}{1 + A'\beta} = 8.43 \Omega$$

Open and closed 3 dB frequencies:

$$f_{L3dB, closed} = \frac{f_{L3dB, open}}{1 + A'B} = 0.399 \text{ Hz}$$

$$f_{H3dB, closed} = \frac{f_{H3dB, open}}{1 + A'B} = 670.2 \text{ kHz}$$

The circuit in below in figure 3.3 is simulated and the closed loop characteristic values were measured and compared to the calculated values.

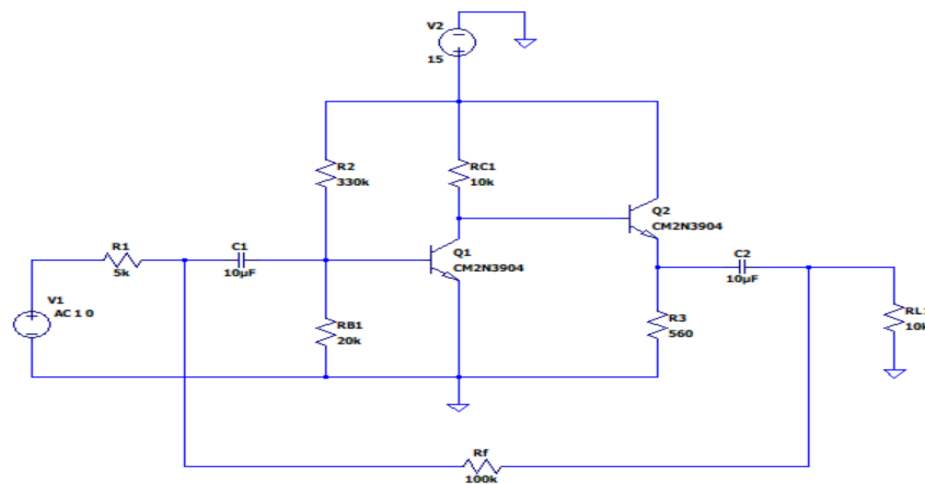


Figure 3.3: Closed loop circuit

	Calculated	Measured
$f_{L3dB}$	399 mHz	499.2 mHz
$f_{H3dB}$	670.2 KHz	679.2 kHz
$R_{in}$	352 $\Omega$	241.1 $\Omega$
$R_{out}$	8.43 $\Omega$	8.456 $\Omega$

Table 3.4: Calculated versus measured closed loop values

3)

The magnitude bode plot for closed loop response by varying values of  $R_f$  is shown in figure 3.4 . The varied values of  $R_f$  are 1 k $\Omega$ , 10 k $\Omega$ , 100 k $\Omega$ , 1 M $\Omega$  and 10 M $\Omega$ . In figure 3.4, the top most graph is 10 M $\Omega$  and the subsequent one is 1 M $\Omega$  and so on.

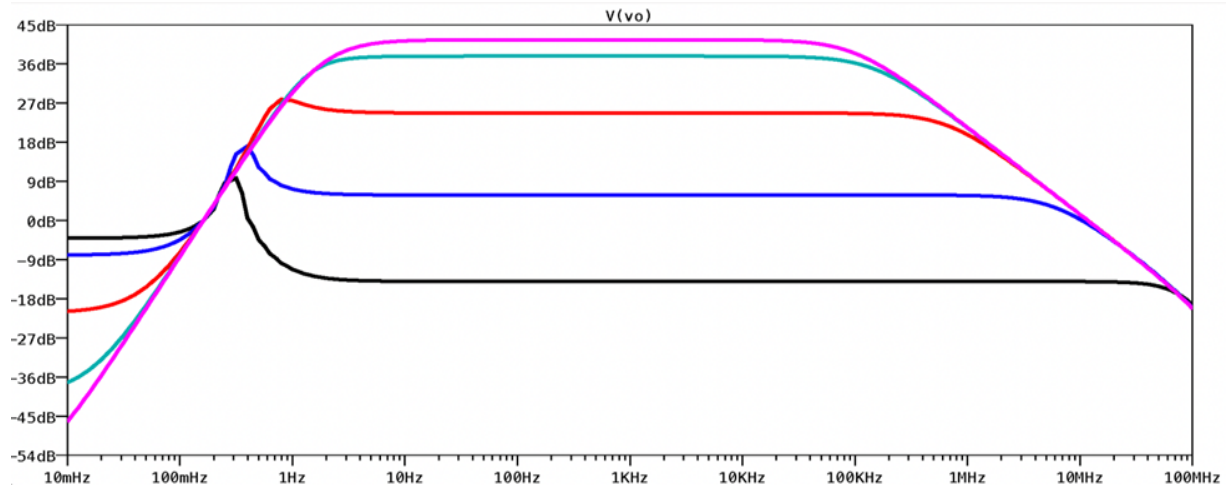


Figure 3.4: Closed loop magnitude plot with varying  $R_f$

The equations to find the measured value of  $\beta$  is shown below:

$$A_f = \frac{A}{1 + A\beta}$$

$$\text{Thus, } \beta = \frac{A' - A_f}{A' A_f}$$

Since the open loop gain stay the same as the past part, the value that need to be calculated from the bode plot is  $A_f$ . Upon measuring the  $A_f$  value from the bod plot, it is noticed that the unit for this is V/V while we need a unit of V/A. Thus, we multiply it by 5 k $\Omega$ . The equation for finding the calculated value of  $\beta$  is shown below:

$$\beta = -\frac{1}{R_f}$$

$R_f$	$A_f$ (kV/A)	Calculated $\beta$	Measured $\beta$
1 k $\Omega$	-9.95	-1 m $\Omega$	-1.001 m $\Omega$
10 k $\Omega$	-9.98	-100 $\mu\Omega$	-100.270 $\mu\Omega$
100 k $\Omega$	-85.9	-10 $\mu\Omega$	-10.021 $\mu\Omega$
1 M $\Omega$	-389.1	-1 $\mu\Omega$	-1091 $\mu\Omega$
10 m $\Omega$	-598.9	-0.1 $\mu\Omega$	-0.09781 $\mu\Omega$

Table 3.5: calculated and measured  $\beta$  comparison with  $R_f$  varied

As seen from table 3.5 that the measure and calculated  $\beta$  are fairly close to one another. However, it becomes slightly less accurate as the value of  $R_f$  is seen to increase.

4)

The values below were found using the method described in past part.

$R_f$	$R_{if}$	$R_{of}$
<b>10 kΩ</b>	26.461 Ω	1.107 Ω
<b>100 kΩ</b>	241.159 Ω	8.462 Ω
<b>1 MΩ</b>	1.308 kΩ	37.30 Ω

Table 3.6: Input and output resistance at 1 kHz with varying values of  $R_f$

To estimate the amount of feedback,  $1 + A\beta$ , one can utilize the connection between input and output impedance and the amount of feedback in the shunt-shunt configuration.

$$R_{if} = \frac{R_i}{1 + A\beta}, \quad R_{of} = \frac{R_o}{1 + A\beta}$$

$$\text{So, } 1 + A\beta = \frac{R_i}{R_{if}} = \frac{R_o}{R_{of}}$$

For the predicted values we use the  $\beta$  values from part 2 and the open loop gain  $A = -631.6 \text{ kV/A}$ .

$R_f$	Predicted AOF	Measured AOF ( $R_{if}$ )	Measured AOF (from $R_{of}$ )
<b>10 kΩ</b>	64.956	71.971	62.371
<b>100 kΩ</b>	7.309	10.01	8.312
<b>1 MΩ</b>	1.643	1.005	1.879

Table 3.7: Values of AOF

As noticed from table 3.7, the predicted and measured value of AOF are more closer to each other for larger values of  $R_f$  compared to smaller ones.

5)

The desensitivity factor can be found using the following equation.

$$\frac{dA_f}{dA} = \frac{1}{(1 + A\beta)^2} \longrightarrow \frac{dA_f}{A_f} = \frac{1}{(1 + A\beta)} \times \frac{dA}{A}$$

$$\therefore \text{desensitivity factor} = 1 + A\beta$$

From the equation of the desensitivity factor, we can understand that as  $R_f$  equates to infinity,  $\beta=0$ . Thus, the desensitivity factor equals 1. Table 3.8 and 3.9 shows the gain by varying RC when  $R_f$  equates to infinity and when  $R_f$  equates to 100 kilohms.

$R_C$ (k $\Omega$ )	A(V/V)
9.9	-126.765
10	-127.497
10.1	-128.086

Table 3.8: table of voltage gain with varied  $R_C$  and equating  $R_f$  equating to infinity

$R_C$ (k $\Omega$ )	A(V/V)
9.9	-17.241
10	-17.250
10.1	-17.258

Table 3.8: table of voltage gain with varied  $R_C$  and equating  $R_f$  equating to 100 k $\Omega$

From prior parts, we can calculate our theoretical desensitivity factor:

$$1 + (-631.6 \times 10^3 \times -10 \times 10^{-6}) = 7.316$$

Using the values obtaining in table 3.8 and 3.9, we can calculate the desensitivity factor and compare it with our theoretical value. The calculation for this shown below.

$$\Delta A = \frac{(-127.497 + 126.765) + (-128.086 + 127.497)}{2} = -0.6605$$

$$\Delta A_f = \frac{(-17.298 + 17.199) + (-17.298 + 17.259)}{2} = -0.0085$$

$$\text{desensitivity factor} = \sqrt{\frac{\Delta A}{\Delta A_f}} = 7.91$$

The desensitivity factor calculated using values in part 2 and 3 are 7.316 and the desensitivity factor calculated in this part is 7.91. From the two numbers, it is observed that the desensitivity factor in both parts theoretical and measured are fairly close to each other.



**Discussion:**

This exercise provided a comprehensive exploration of the dynamics and characteristics of a feedback circuit featuring a two-stage cascaded transistor amplifier. Through practical implementation and testing, key insights were gained into the intricacies of DC bias adjustments for optimizing open-loop gain, the influence of feedback network parameters on amplifier performance, and the behavior of closed-loop frequency responses under various configurations. Analysis of transistor parameters, such as  $g_m$ ,  $r_\pi$ , and  $h_{FE}$  offered a deeper understanding of amplifier behavior. The exercises further honed skills in measuring and calculating key amplifier parameters, interpreting frequency response plots, and assessing the effects of feedback on both input and output resistances, thereby enhancing overall comprehension of amplifier design and behavior in practical applications.

Additionally, it is observed that when employing smaller values for  $R_f$ , the amplifier gain is larger than at the mid-band. This may be due to the reason that for smaller values of  $R_f$ , a lesser negative feedback gain is obtained, increasing the overall gain of the system.

**References:**

- [1] Miniproject 4 handout
- [2] ELEC 301 course notes